

The following features of the [ADuC7061](#) are used in this application:

- Primary 24-bit Σ - Δ ADC with programmable gain amplifier (PGA): The PGA is set for a gain of 32 in the software for this application.
- Programmable excitation current sources for forcing a controlled current through the RTD: The dual current sources are configurable in 200 μ A steps from 0 μ A to 2 mA. For this example, a 200 μ A setting was used.
- External voltage reference for the ADC in the [ADuC7061](#): For this application, we used a ratiometric setup where an external reference resistor (R_{REF}) is connected across the external V_{REF+} and V_{REF-} pins. Alternatively, an internal 1.2 V reference is provided in the [ADuC7061](#).
- ARM7TDMI® core: The powerful 16-/32-bit ARM7 core with integrated 32 kB flash and SRAM memory runs the user code that configures and controls the ADC, processes the ADC conversions from the RTD, and controls the communications over the UART/USB interface.
- UART: The UART was used as the communication interface to the host PC.
- Two external switches are used to force the part into its flash boot mode: By holding S1 low and toggling S2, the [ADuC7061](#) will enter boot mode instead of normal user mode. In boot mode, the internal flash may be reprogrammed through the UART interface.

The RTD used in the circuit is a platinum 100 Ω RTD, model number [Energcorp PCS 1.1503.1](#). It is available in a 0805 surface-mount package. This RTD has a temperature variation of 0.385 Ω /°C.

Note that the reference resistor, R_{REF} , should be a precision 5.62 k Ω (\pm 0.1%).

The USB interface to the [ADuC7061](#) is implemented with an [FT232R UART to USB transceiver](#), which converts USB signals directly to the UART.

In addition to the decoupling shown in Figure 1, the USB cable itself should have a ferrite for added EMI/RFI protection. The ferrite beads used in the circuit were Taiyo Yuden, #BK2125HS102-T, which have an impedance of 1000 Ω at 100 MHz.

The circuit must be constructed on a multilayer PC board with a large area ground plane. Proper layout, grounding, and decoupling techniques must be used to achieve optimum performance (see [Tutorial MT-031, Grounding Data Converters and Solving the Mystery of "AGND" and "DGND,"](#) [Tutorial MT-101, Decoupling Techniques](#), and the [ADuC7061 Evaluation Board](#) layout).

CODE DESCRIPTION

The source code used to test the attached circuit can be downloaded as a zip file at www.analog.com/cn0075_source.

The UART is configured for a baud rate of 9600, 8 data bits, no parity, no flow control. If the circuit is connected directly to a PC, a communication port viewing application such as HyperTerminal can be used to view the results sent by the program to the UART. See Figure 2. The source code is commented to make it easier to understand and manipulate.

For details on linearization and maximizing the performance of the circuit, refer to [Application Note AN-0970, RTD Interfacing and Linearization Using an ADuC706x Microcontroller](#).

```

9600 - HyperTerminal
File Edit View Call Transfer Help
[Icons]
RTD value : +110.858ohms,
Temperature : +28.20C,
ADC0 Result (hex) : A22B83,
RTD value : +110.858ohms,

Temperature : +28.21C,
ADC0 Result (hex) : A22C35,
RTD value : +110.860ohms,

Temperature : +28.21C,
ADC0 Result (hex) : A22C42,
RTD value : +110.860ohms,

Temperature : +28.21C,
ADC0 Result (hex) : A22BBA,
RTD value : +110.859ohms,

Disconnected AN51W 9600 B-N-1 SCROLL CAPS NUM Capture PrintEcho
08283-002

```

Figure 2. Output of HyperTerminal Communication Port Viewing Application

COMMON VARIATIONS

The ADP7102 regulator can be used as a newer alternate to the [ADP3333](#). If more GPIO pins are required on the microcontroller, the [ADuC7060](#), which comes in a 48-LFCSP or 48-LQFP package, is another option. Note that the ADuC7060/ADu7061 can be programmed or debugged via a standard JTAG interface. For a standard UART to RS-232 interface, the FT232R transceiver could be replaced with a device such as the [ADM3202](#), which requires a 3 V volt power supply.

LEARN MORE

[ADIsimPower Design Tool.](#)

[CN-0075 Circuit Test Source Code File..](#)

Kester, Walt. 1999. *Sensor Signal Conditioning*. Analog Devices. Chapter 7, "Temperature Sensors."

Kester,Walt. 1999. *Sensor Signal Conditioning*. Analog Devices. Chapter 8, "ADCs for Signal Conditioning."

Looney, Mike. *RTD Interfacing and Linearization Using an ADuC706x Microcontroller*. AN-0970 Application Note. Analog Devices.

[MT-022 Tutorial, ADC Architectures III: Sigma-Delta ADC Basics](#). Analog Devices.

[MT-023 Tutorial, ADC Architectures IV: Sigma-Delta ADC Advanced Concepts and Applications](#). Analog Devices.

[MT-031 Tutorial, Grounding Data Converters and Solving the Mystery of "AGND" and "DGND."](#) Analog Devices.

[MT-101 Tutorial, Decoupling Techniques](#). Analog Devices.

Data Sheets and Evaluation Boards

[ADuC7061 Data Sheet.](#)

[ADuC7061 Evaluation Kit.](#)

[ADM3202 UART to RS232 Transceiver Data Sheet.](#)

[ADP7102 Data Sheet.](#)

[ADP3333 Data Sheet.](#)

REVISION HISTORY

7/13—Rev. 0 to Rev. A

Changes to Devices Connected/Referenced Section..... 1

Changes to Common Variations Section and Data Sheets and

Evaluation Board..... 3

7/09—Revision 0: Initial Version

(Continued from first page) "Circuits from the Lab" are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the "Circuits from the Lab" in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the "Circuits from the Lab". Information furnished by Analog Devices is believed to be accurate and reliable. However, "Circuits from the Lab" are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any "Circuits from the Lab" at any time without notice, but is under no obligation to do so. Trademarks and registered trademarks are the property of their respective owners.

©2009–2013 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.
CN08283-0-7/13(A)



www.analog.com